

Functional Notation

Addendum to Chapter 4

Logic Notation Systems

- ▶ We have seen three different, but equally powerful, notational methods for describing the behavior of gates and circuits:
 - ▶ Boolean expressions
 - ▶ logic diagrams
 - ▶ truth tables

Recall that...

- ▶ **Boolean expressions** are expressions in Boolean algebra, a mathematical notation for expressing two-valued logic.

This algebraic notation is an elegant and powerful way to demonstrate the activity of electrical circuits.

Recall further that...

- ▶ **Logic diagram** A graphical representation of a circuit

Each type of gate is represented by a specific graphical symbol.

- ▶ **Truth table** A table showing all possible input value and the associated output values.

A Fourth System

In addition to these three, there is another widely used system of notation for logic.

Functional Notation

Functional Notation

- ▶ Uses a function name followed by a list of arguments in place of the operators used in Boolean Notation.
- ▶ For example:
 A' becomes NOT(A)

Functional Equivalents

Boolean Notation	Functional Notation
$X=A'$	$X=\text{NOT}(A)$
$X=A + B$	$X=\text{OR}(A,B)$
$X=A \cdot B$	$X=\text{AND}(A,B)$
$X=(A + B)'$	$X=\text{NOT}(\text{OR}(A,B))$
$X=(A \cdot B)'$	$X=\text{NOT}(\text{AND}(A,B))$

XOR

If/when the XOR function is not available, it must be defined in terms of the 3 logic primitives: AND, OR, and NOT

Recall its explanation:

“one or the other but not both”

In Boolean Notation this becomes:

$$X = (A + B) \cdot (A \cdot B)'$$

In Functional Notation:

$$X = \text{AND}(\text{OR}(A, B), \text{NOT}(\text{AND}(A, B)))$$

XOR

The truth table for XOR reveals a hint for simplifying or expression.

Note that XOR is false (0) when A and B are the same, and true (1) when they are different.

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

XOR


So XOR can be expressed very simply as:

$$X = \text{NOT}(A = B)$$

or

$$X = A < > B$$


Consider this familiar circuit

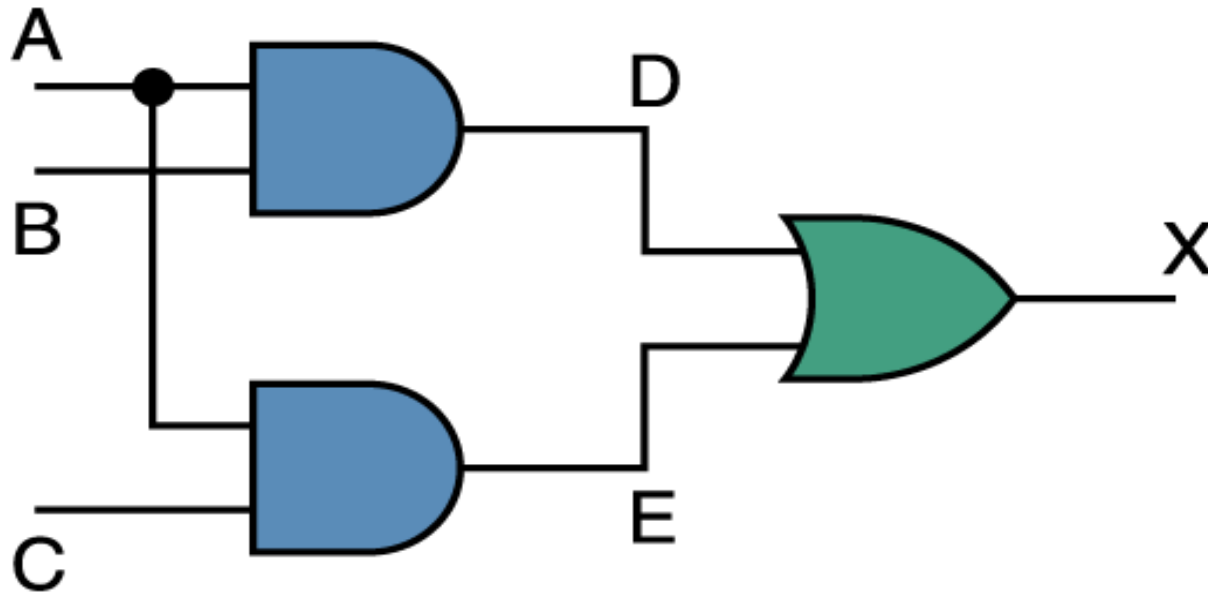

$$X = (AB + AC)$$

How will this expression look in functional notation?


Equivalent expressions

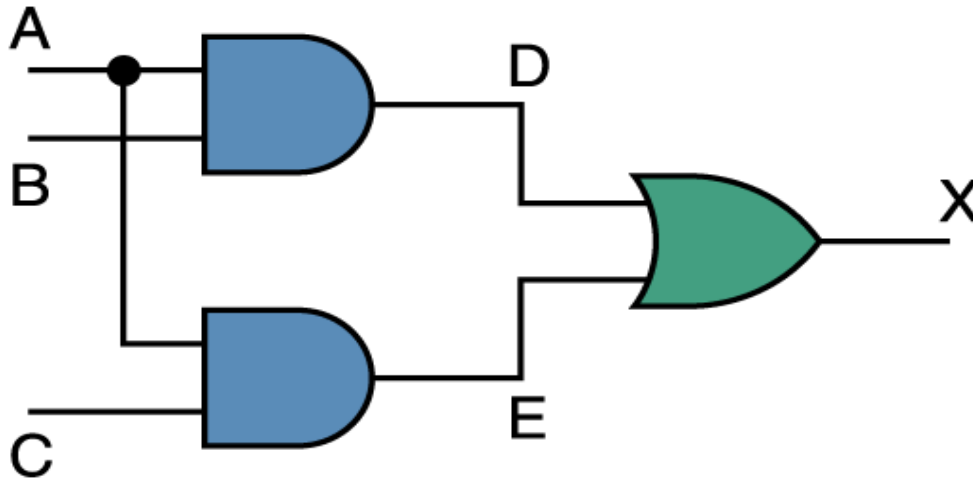

$$X = (AB + AC)$$

$$X = \text{OR}(\text{AND}(A, B), \text{AND}(A, C))$$

The equivalent circuit

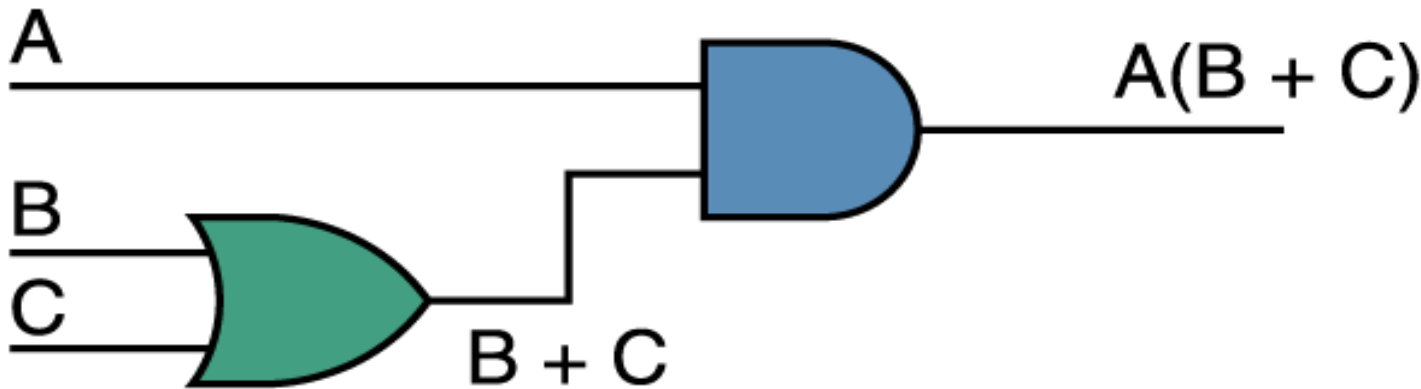

$$X = A (B + C)$$

$$X = \text{AND}(A, \text{OR}(B, C))$$